SM ₁	I211	RF	Mo	du	le
-----------------	------	----	----	----	----

User's Guide



Table of Contents

1 Introduction	
2 Getting Started	3
3 Schematics	4
4 Layout	4
5 BOM	5
6 References	5
Table of Figures	
Figure 1: SM1211 Overview (top view)	3
Figure 1: SM1211 Overview (top view)	4
Figure 1: SM1211 Overview (top view)	4 4
Figure 1: SM1211 Overview (top view)	

1 Introduction

The purpose of this tool is to provide a development platform of the SX1211. User can build his application prototype by simply connecting the module to his target microcontroller and start developing his application software. The SM1211 module integrates the SX1211 reference design (chip + external components) plus miscellaneous useful connectors.

Note that this module is also used for the SX1211 Starter Kit.

2 Getting Started

As illustrated in figure below, the SM1211 integrates several parts:

- Ref design: This section includes the chip but also all the external components in an optimized BOM and form factor. When user wants to incorporate the SX1211 on his PCB, it is strongly recommended that this reference design (i.e. schematics, placement, layout, BOM, etc...) is copied "as is" in final application board to guarantee optimum performance and lowest development time and design effort.
- uC connector: to connect the RF chip's control lines to the uC. (Cf SX1211 datasheet for uC connections guidelines).
- SMA connector: SMA Cable or antenna connection. Each board is delivered with its ¼ wave SMA antenna.
- **VDD jumper**: to monitor current consumption and/or apply independent power supply to the module. When VDD jumper is on, RF module's power supply should be supplied on the uC connector.

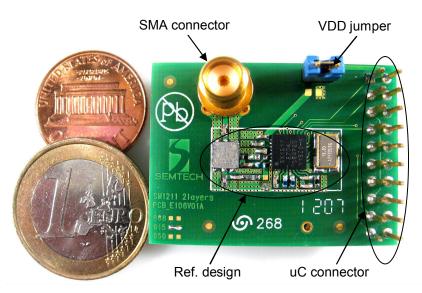


Figure 1: SM1211 Overview (top view)

Software drivers are available in the API TN8000.18 on Semtech's website. These are implemented on Semtech's XE8000 microcontrollers but are written in C and hence easily portable to other targets.

3 Schematics

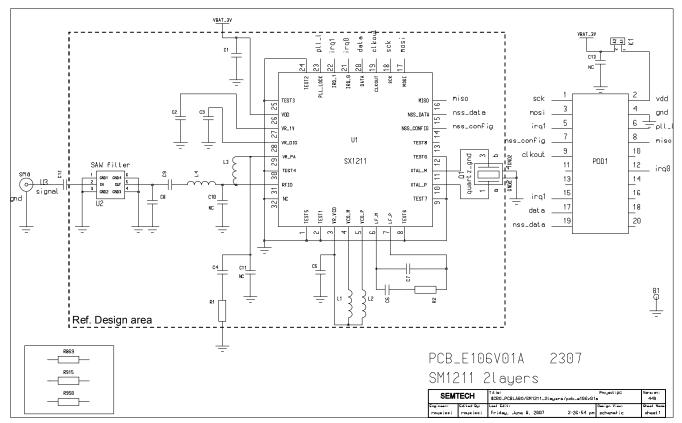


Figure 2: SM1211 Schematics

C12 is a DC blocker protection for the SAW filter. It has been added for debug/dev purposes, it is not needed for direct antenna connection.

Please note that C10 and C11 are not used.

4 Layout

As illustrated in figures below, the layout has the following characteristics:

- √ very compact ref design (9x19mm) => can be easily inserted even on very small PCBs.
- ✓ standard PCB technology (2 layers, 1.6mm, std vias & clearance) => low cost
- ✓ performance quasi insensitive to dielectric thickness => quasi zero effort portability to other PCB technology (thickness, # of layers, etc...)

The layers description is illustrated in figure below.

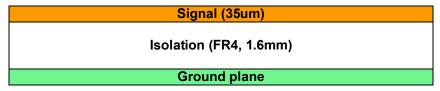


Figure 3: SM1211 Layers Description (cut view)

The layout itself is illustrated in figure below. Please contact Semtech for gerber files.

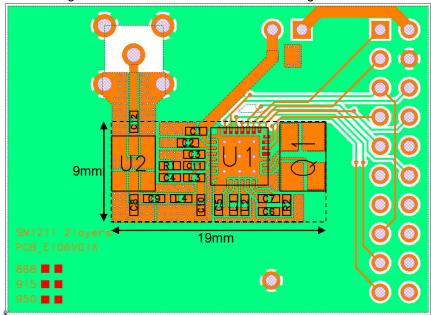


Figure 4: SM1211 Layout (top view)

5 BOM

Ref	Value		Tol (+/-)	Techno	Size	Comment	
	868MHz	915MHz					
U1 -	SX1211		-	Transceiver IC	TQFN-32	-	
U2	869MHz	915MHz	-	SAW Filter	3.8*3.8mm	Part# Temex S142/S110	
Q1	12.8MHz		15ppm at 25°C	AT-cut	5.0*3.2mm	Fundamental, Cload=15pF	
1			20ppm over -40/+85°C			Part# Siward SX5032	
			2ppm/year max.				
R1	1Ω		1%	-	0402	PA regulator	
R2	6.8kΩ		1%	-	0402	Loop filter	
C1	1uF		15%	X5R	0402	VDD decoupling	
C2	1uF		15%	X5R	0402	Top regulator decoupling	
C3	220nF		10%	X7R	0402	Digital regulator decoupling	
C4	47nF		10%	X7R	0402	PA regulator decoupling	
C5	100nF		10%	X7R	0402	VCO regulator decoupling	
C6	10nF		10%	X7R	0402	Loop Filter	
C7	680pF		10%	X7R	0402	Loop Filter	
C8	1.8pF		0.25pF	NPO	0402	Matching	
C9	22pF		5%	NPO	0402	DC block and L4 adjust	
L1, L2	8.2nH	6.8nH	0.2nH	Wire wound	0402	VCO tank inductors	
L3	100nH		5%	Wire wound	0402	PA Choke	
L4	8.2nH		5%	Multilayer	0402	Matching	
C10,C11	NC		-	I -	0402	-	
C12*	47pF		5%	NPO	0402	DC block	

^{*}Not part of the ref. design (not required for direct antenna connection).

Figure 5: SM1211 BOM

6 References

- > [1] SX1211 Datasheet
- > [2] TN8000.18 API

© Semtech 2007

All rights reserved. Reproduction in whole or in part is prohibited without the prior written consent of the copyright owner. The information presented in this document does not form part of any quotation or contract, is believed to be accurate and reliable and may be changed without notice. No liability will be accepted by the publisher for any consequence of its use. Publication thereof does not convey nor imply any license under patent or other industrial or intellectual property rights. Semtech. assumes no responsibility or liability whatsoever for any failure or unexpected operation resulting from misuse, neglect improper installation, repair or improper handling or unusual physical or electrical stress including, but not limited to, exposure to parameters beyond the specified maximum ratings or operation outside the specified range.

SEMTECH PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT APPLICATIONS, DEVICES OR SYSTEMS OR OTHER CRITICAL APPLICATIONS. INCLUSION OF SEMTECH PRODUCTS IN SUCH APPLICATIONS IS UNDERSTOOD TO BE UNDERTAKEN SOLELY AT THE CUSTOMER'S OWN RISK. Should a customer purchase or use Semtech products for any such unauthorized application, the customer shall indemnify and hold Semtech and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs damages and attorney fees which could arise.

Contact Information

Semtech Corporation Advanced Communications and Sensing Products Division 200 Flynn Road, Camarillo, CA 93012 Phone (805) 498-2111 Fax: (805) 498-3804